



# Electronics II

## Lecture 03 BJT re Equivalent Model

Muhammad Tilal  
Department of Electrical Engineering  
CIIT Attock Campus

The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited. The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden.



## Previous Lecture

- Amplifying Action in AC Domain.
- BJT Transistor Modeling.
- Important Amplifier Parameters using Two Port System
  - Input Impedance.
  - Output Impedance.




## Session Overview

<b>Topic</b>	BJT $r_e$ Equivalent Model
<b>Concepts</b>	Voltage Gain, Current Gain, Phase relationship  re Equivalent Model for <ul style="list-style-type: none"> <li>▪ Common Base Configuration.</li> <li>▪ Common Emitter Configuration.</li> <li>▪ Common Collector Configuration.</li> </ul>
<b>Recommended Reading</b>	Sections 7.4 & 7.5 of [1]
<b>Keywords</b>	$r_e$ , BJT, Common Base, Common Emitter, Common Collector, Equivalent Model.



## Voltage Gain, $A_v$

- Small signal ac voltage gain is given as  
 $A_v = V_o/V_i$ .
  - If load is not connected to the output, then this voltage gain is called “no load voltage gain” and calculated as  
 $A_{VNL} = V_o/V_i |_{R_L = \text{infinite}}$
  - Normally for transistor amplifiers no load voltage gain is greater than the loaded voltage gain.
- $V_i =$
  - $V_i/V_s =$
  - $A_{Vs} = V_o/V_s =$
  - $A_{Vs} =$
  - Typical Magnitude of voltage gain ?

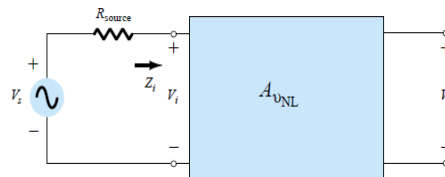


Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# Voltage Gain, $A_v$

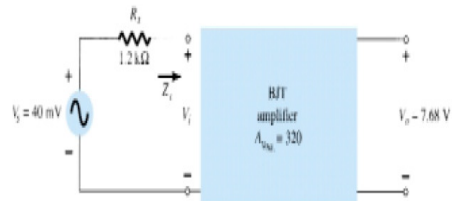- Example 7.3 (Boylestad):
- For the given BJT amplifier, determine
  - $V_i =$
  - $I_i =$
  - $Z_i =$
  - $A_{vs} =$



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# Current Gain, $A_i$

- The small signal ac current gain is defined as
 
$$A_i = I_o / I_i$$
- For BJT amplifiers, typical range of  $A_i$  exceed from 1 to 100.
- For the given network
 
$$I_i = V_i / Z_i$$

$$I_o = -V_o / R_L$$



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



## Phase Relationship

- For a typical transistor amplifier at frequencies at which the effects of reactive elements can be ignored, the input and output signals are either 180 degrees out of phase or in phase.




## $r_e$ Transistor Model

- This model employs a diode and controlled current source to represent the behavior of a transistor.
- Current controlled current source is the one in which the parameters of the current source are controlled by a current.
- The  $r_e$  transistor model will be investigated for the following three configurations of the BJT amplifiers.
  - Common Base Configuration.
  - Common Emitter Configuration.
  - Common Collector Configuration.


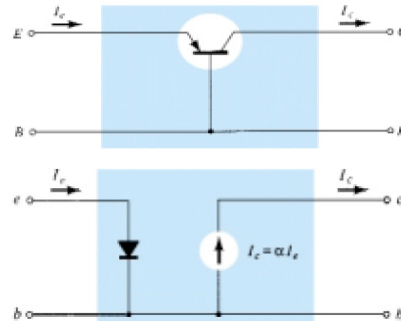
# Common Base Configuration


- A pnp transistor is employed to derive the  $r_e$  model for common base configuration.
- It is depicted in a way to replicate the two port network.
- The forward biased pn junction is replaced by a diode.
- A current source is connected in order to represent the collector current  $I_c$ .
- AC resistance of diode can be determined by
- $r_{ac} = 26mV/I_D$ .  $r_e = 26mV/I_E$



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# Common Base Configuration

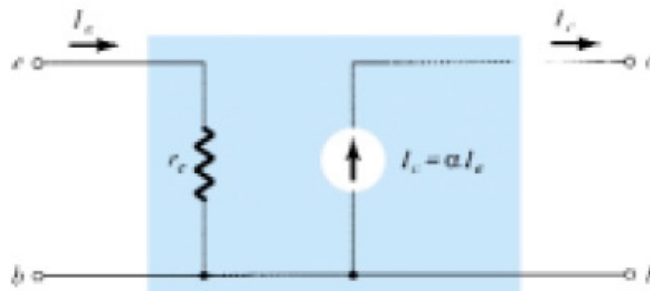

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.