



Electronics II

Lecture 08 FET Small Signal Analysis

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited. The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden.



Previous Lecture

- BJT Small Signal Analysis
 - Small Signal Analysis of CE Emitter Bias Configuration.
 - Small Signal Analysis of Emitter Follower Configuration.
 - Small Signal Analysis of Common Base Configuration.



Session Overview

Topic	FET Small Signal Analysis
Concepts	Trans- conductance, Input Impedance, Output Impedance, FET AC Equivalent Circuit, JFET Fixed Bias Configuration Small Signal Analysis.
Recommended Reading	Sections 9.1, 9.2 & 9.3 of [1]
Keywords	Emitter Follower, Common Base, Small Signal, BJT, Fixed Bias.



FET Amplifiers

- Good Voltage Gain.
- High Input Impedance.
- Less power consumption.
- Work with wide range of frequencies.
- Small size and weight.
- Trans- conductance factor (g_m) is the counterpart of amplification factor (β).
- Current gain: Undefined (Why)
- Common Source
 - Most popular.
 - Characterized by inverted amplified signal.
- Common Drain.
 - Characterized by unity gain and no inversion.
- Common Gate.
 - Characterized by gain with no inversion.
- Input Impedance is very high.
- Output Impedance is comparable to that of BJT.



FET Small Signal Model

- FET is a voltage controlled device, so the relationship between the V_{GS} and I_D is defined as

$$\Delta I_D = g_m \Delta V_{GS}$$


where

I_D = controlled current.

V_{GS} = Controlling Voltage.

- g_m is called trans-conductance, where the term trans is used to describe the relationship between input and output.

 - $g_m = \Delta I_D / \Delta V_{GS}$
- $g_m = m = \Delta y / \Delta x = \Delta I_D / \Delta V_{GS}$




$$g_m \equiv \frac{\Delta I_D}{\Delta V_{GS}} \text{ (Slope at Q-point)}$$

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



FET Small Signal Model

 - Example 9.1 (Boylestad):** Determine the magnitude of g_m for a JFET with $I_{DSS} = 8\text{mA}$ and $V_P = -4\text{V}$ at following DC bias points
 - $V_{GS} = -0.5\text{V}$.
 - $V_{GS} = -1.5\text{V}$.
 - $V_{GS} = -2.5\text{V}$.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




FET Small Signal Model

- **Mathematical Definition of g_m :**
- The derivative of a function at a point is equal to the slope of the tangent line drawn at that point.
- $g_m = (2I_{DSS}/|V_P|)[1 - V_{GS}/V_P]$
- $g_{m0} = (2I_{DSS}/|V_P|)$
- $g_m = g_{m0}[1 - V_{GS}/V_P]$



FET Small Signal Model

 - Example 9.2 (Boylestad): For the JFET of Example 9.1,
 - Find the max. value of g_m .
 - Find the value of g_m at each operating point of Example 9.1 using mathematical formula and compare with the graphical results.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



FET Small Signal Model

- g_m vs V_{GS}

 


Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



FET Small Signal Model

- Input Impedance
 $Z_i(\text{FET}) = \infty \Omega$
 Typical Values
 JFET = $1000 M\Omega$
 MOSFET = 10^{12} to $10^{15} \Omega$
- Output Impedance
 $Z_o(\text{FET}) = r_d = 1/y_{os}$
 $r_d = (\Delta V_{DS} / \Delta I_D) |_{V_{GS} = \text{constant}}$

 


Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




FET Small Signal Model

 - *Example 9.5(Boylestad):*
Determine the output Impedance for the given FET curves for
 - $V_{GS} = 0V$ (at $V_{DS} = 8V$).
 - $V_{GS} = -2V$ (at $V_{DS} = 8V$).



FET Small Signal Model

 - FET AC Equivalent Circuit
- I_d represented as a voltage controlled current source $g_m V_{gs}$ with 180 degrees phase shift.
- Input impedance is represented as an open circuit at input terminals.
- Output impedance is represented by r_d from drain to source.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



FET Small Signal Model

 
- *Example 9.6 (Boylestad):*
Sketch FET ac Equivalent Model for $y_{fs}= 3.8\text{mS}$ and $y_{os}= 20\mu\text{S}$.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




JFET Fixed Bias Configuration

 

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



JFET Fixed Bias Configuration

 

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




JFET Fixed Bias Configuration

 - *Example 9.7 (Boylestad):* The given fixed bias configuration has an operating point defined by $V_{GSQ} = -2V$, $I_{DQ} = 5.625mA$ and $I_{DSS} = 10mA$ and $V_P = -8V$.

Assume $y_{os} = 40\mu S$, determine

- g_m
- Z_i
- Z_o
- A_v
- A_v (ignoring the effects of r_d)



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.