



# Electronics II

Lecture 09  
Multistage Amplifiers  
Part 01

Muhammad Tilal  
Department of Electrical Engineering  
CIIT Attock Campus

The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited. The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden.



## Previous Lecture

- FET Small Signal Analysis
  - AC Equivalent Circuit and related Parameters .
  - Small Signal Analysis of JFET Fixed Bias Configuration.



## Session Overview

<b>Topic</b>	Multistage Amplifiers
<b>Concepts</b>	Cascade Connection, Cascode Connection.
<b>Recommended Reading</b>	Sections 12.1,12.2, 12.3 of [1].
<b>Keywords</b>	Cascade, Cascode.




## Multistage/ Compound Configurations

- For various practical purposes, the single stage amplifiers are not sufficient.
- Multistage/ compound configurations are employed to enhance the functionality and suitability for different purposes.
- Most important of these configurations are considered for study here. These include
  - Cascade Connection
    - Amp. Stages in series.
  - Cascode Connection
    - Amp. Stages on top of each other.
  - Darlington Pair.
    - Multiple stages connected to operate as a single transistor.


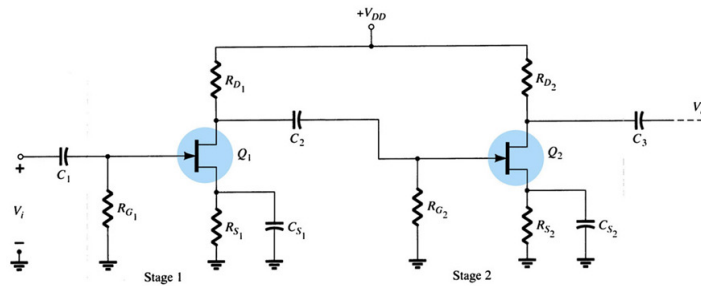
# Cascade Connection

- It's a series connection where the output of one stage acts as an input to the next stage.
- **Phase relationship of input & output?**
- The total voltage gain of cascade connection is the product of the individual stage gains i.e.  $A_v = A_{v1} * A_{v2}$
- $Z_i = R_{G1}$      $Z_o = R_{D2}$




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



# Cascade Connection

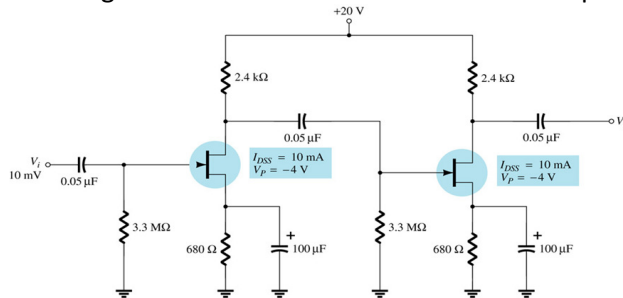- *Example 12.1 (Boylestad):*  
Calculate DC Bias, voltage gain, input impedance, output impedance and output voltage for the given cascaded amplifier. Also calculate the load voltage if a 10kΩ load is connected to the output.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.


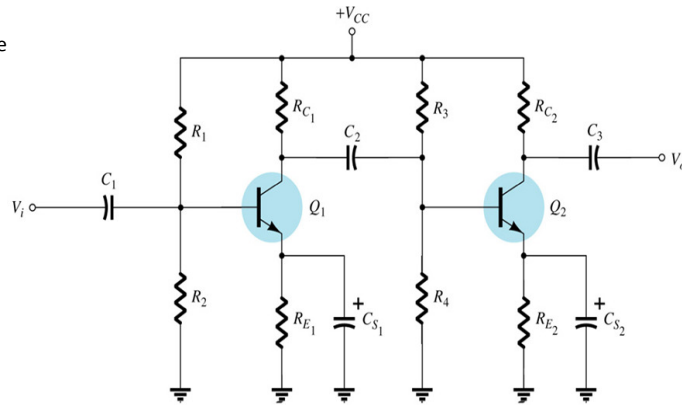
# BJT Cascade Amplifier

- $A_v = -(R_C \parallel R_L)/r_e$
- $Z_i = R_1 \parallel R_2 \parallel \beta r_e$
- $Z_o = R_C \parallel r_o$




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# BJT Cascade Amplifier

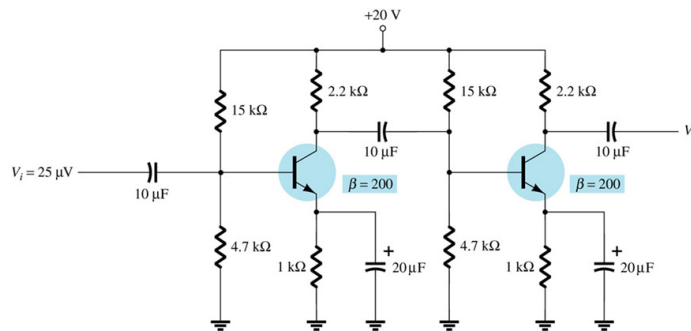- *Example 12.2 (Boylestad):*  
Calculate voltage gain, input impedance, output impedance and output voltage for the given cascaded BJT amplifier. Also calculate the load voltage if a 10kΩ load is connected to the output.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# BJT Cascade Amplifier

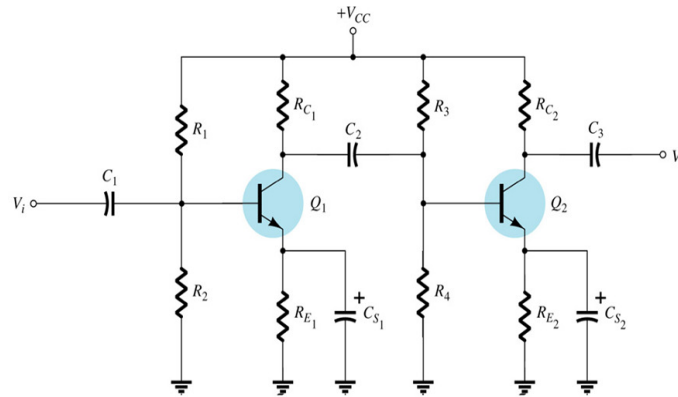- *Task:* Calculate  $Z_o$  of stage 01 and  $Z_{in}$  of stage 02 for the given configuration.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



# FET-BJT Cascade Amplifier

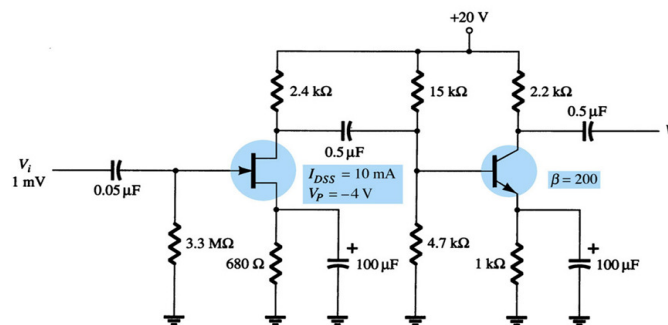
- *Example 12.3 (Boylestad):*  
Calculate input impedance, output impedance, voltage gain and output voltage for the given cascade amplifier using the DC bias conditions calculated in Example 12.1 & 12.2.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



# Cascode Connection

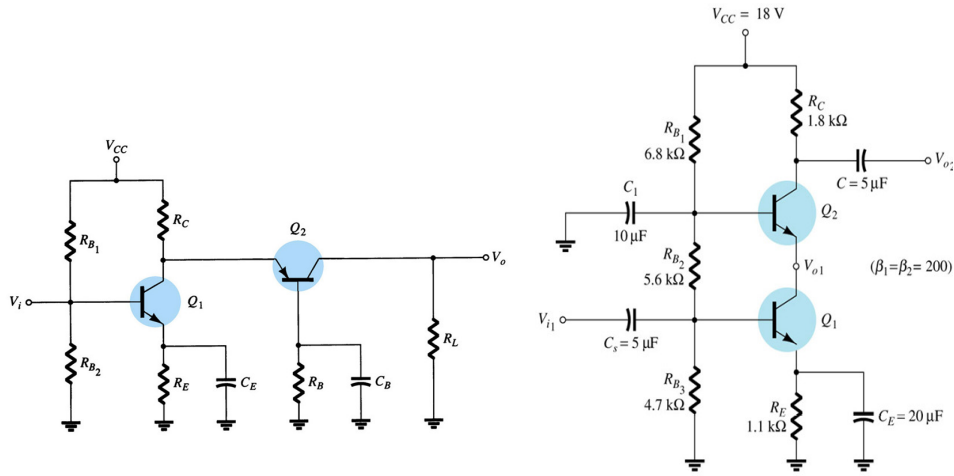


Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# Cascode Connection

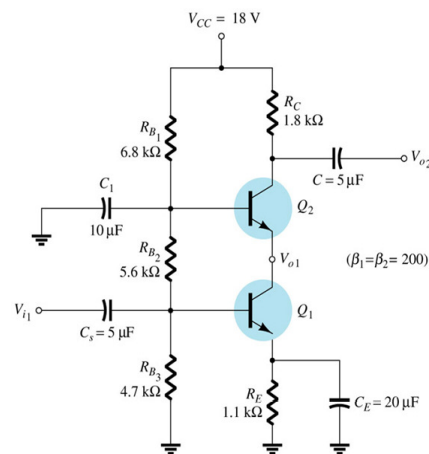- *Example 12.4(Boylestad):* Calculate the voltage gain for the given cascode amplifier.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



# References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.