



Electronics II

Lecture 13 Operational Amplifiers- Applications

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited. The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden.



Previous Lecture

- Operational Amplifier Amplifier
 - Ideal Op-amp.
 - Modes of Operation.
 - Common Mode Rejection Ratio



Session Overview


Topic	Operational Amplifiers (Op Amp)- Applications
Concepts	Voltage Summation, Voltage Subtraction.
Recommended Reading	Section 13.1, 13.2 & 13.4 of [1] Section 8-2 of [2].
Keywords	Op Amp, Single Ended, Double Ended, Common Mode, Summation, Subtraction.



Op Amp

- *Example 13.1 (Boylestad):* Calculate CMRR for the given circuit.


Solution:

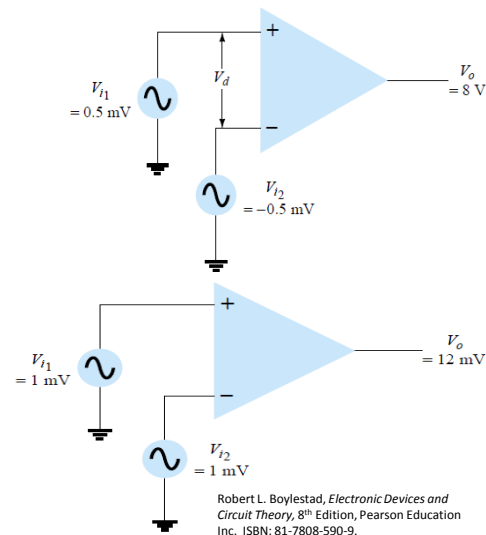




Op Amp

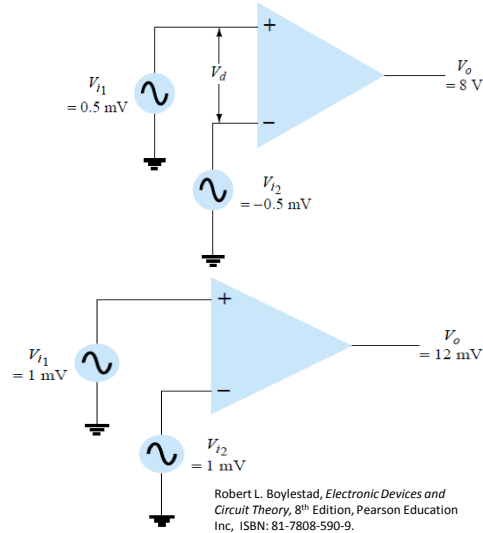- **Example 13.2 (Boylestad):** Determine the output voltage of an op- amp for input voltages of $V_{i1}= 150\mu\text{V}$, $V_{i2}= 140\mu\text{V}$. The amplifier has a differential gain of $A_d= 4000$ and the CMRR is
 - (a) 100
 - (b) 10^5



Voltage Summation (Op- Amp)

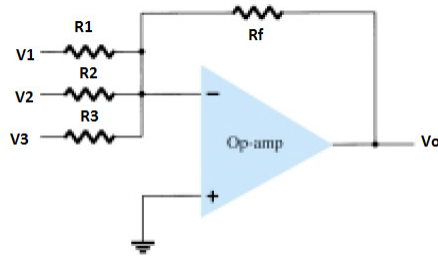
- A linear combination of different voltages using an op- amp is possible.
- An example of such summation could be $2v_1+0.5v_2+4v_3$.
- Such circuit is known as linear combination circuit.
- $v_o= - [(R_f/R_1)*v_1 + (R_f/R_2)*v_2 + (R_f/R_3)*v_3]$
- For $R_1=R_2=R_3=R$
 - $v_o=$
- For $R_f=R$
 - v_o





Voltage Summation (Op- Amp)

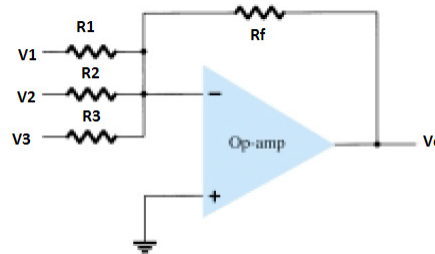- Example 13.5 (Boylestad): Calculate the output voltage for the given values for Voltage summation
 - $V1=+1V, V2=+2V, V3=+3V$
 $R1=500k\Omega, R2= 1M\Omega, R3=1M\Omega$
 - $V1=-2V, V2=+3V, V3=+1V$
 $R1=200k\Omega, R2= 500k\Omega, R3=1M\Omega$
- For $R1=R2=R3=R$
 - $v_o=$
- For $R_f=R$
 - $V_o=$




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Voltage Summation (Op- Amp)


- Non Inverting configuration is also used.
- A bit more complex and cumbersome in terms of precision and calculations.
- Used in the applications where the phase inversion is necessarily not required.
- $v_o= (1+(R_f/R_G)) * ((R_p/R_1)v_1 + (R_p/R_2)v_2 + (R_p/R_3)v_3)$
 - Where $R_p= R_1 || R_2 || R_3$

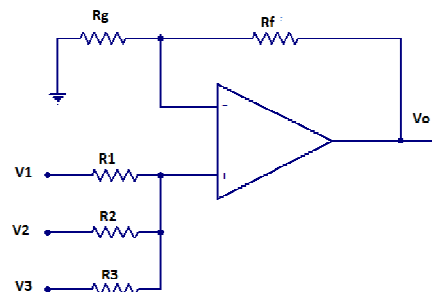



Voltage Subtraction (Op- Amp)

- An op- amp can be used in the differential mode in order to subtract the signals.
- The output voltage is calculated using the superposition
 - $v_o = v_{o1} + v_{o2}$
 - Where $v_{o1} = o/p$ because of v_1 .
 - $v_{o2} = o/p$ because of v_2 .
- This arrangement has some limited functionality to attain a scaled difference of the signals so another arrangement of op- amps is used for the voltage subtraction.

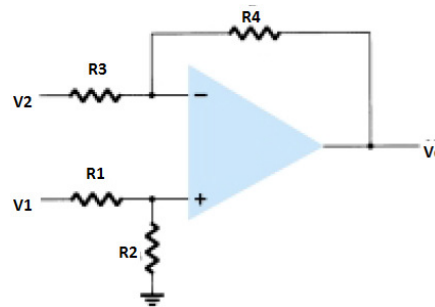

Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3