



Electronics II

Lecture 19 Filters II

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



Previous Lecture

- Filters
 - Basics of Filters.
 - Transfer Function, Magnitude and Phase Response of Filters.
 - Classification of Filters.
 - Important Properties/ Parameters of Filters.



Session Overview



Topic	Filters
Concepts	Important Properties of Filters, Low Pass Filter, High Pass Filter, Band Pass Filter, Band Stop Filter.
Recommended Reading	Section 14-6 of [1] Section 11-5 of [2] Sections 1.0, 1.1, 1.4 of [3]
Keywords	Filter, Low Pass, High Pass, Band Pass, Band Stop, Active, Passive.



Filter Properties

Monotonicity

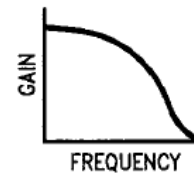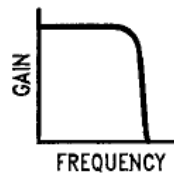- A filter has a monotonic amplitude response if its gain slope never changes sign.
- This implies that gain always increases with the increasing frequency or always decreases with the increasing frequency.
- This is applicable only in high pass and low pass filters whereas band pass and band stop cannot have this property for their total bandwidth.






Filter Properties

Pass Band Ripple

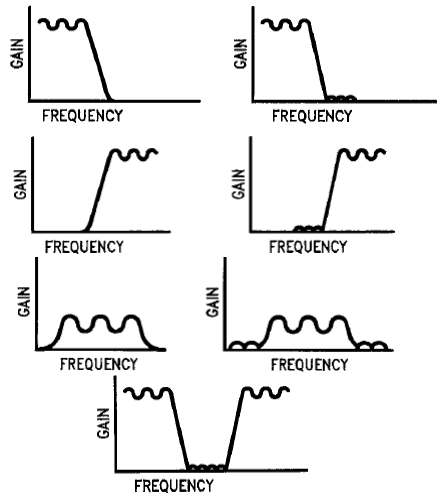- If a filter is not monotonic in its pass band, the transfer function will have fluctuations in the pass band.
- These fluctuations are called as *ripples*. Some systems/applications might not require the monotonicity, but ripple should have a limited value.




Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Filter Properties

Stop Band Ripple

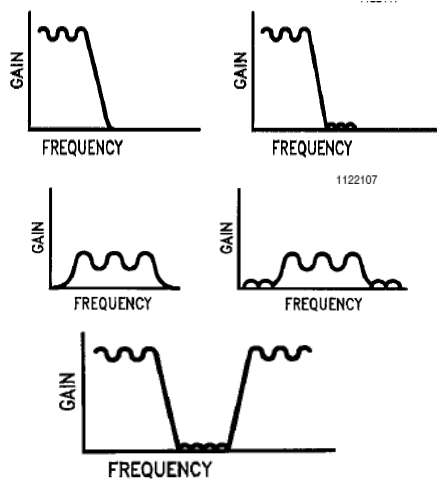- The phenomenon of ripple is also present in the stop band.
- Stop band ripple is usually not of concern if the signal in the stop band is sufficiently attenuated.




Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.




Practical Filter Design and Ideal Filter

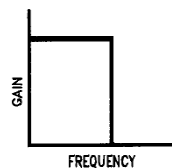- The main goal in filter design is to attain the *ideal filter* characteristics.
- Practically, the ideal filter is not realizable because of certain limitations so an acceptable filter design depends upon various inter related factors which include
 - Amplitude response.
 - Transient response.
 - Physical size and cost of circuit.



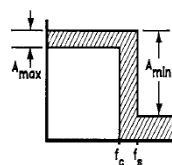(a) "ideal" Low-Pass Filter Response ¹¹²²¹³³





(b) Amplitude Response Limits for a Practical Low-Pass Filter ¹¹²²¹³⁴

Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Practical Filter Design and Ideal Filter

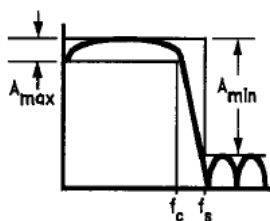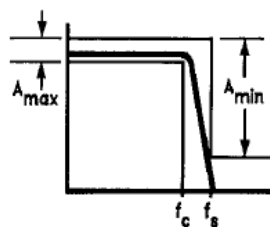- Four parameters are critical in the given figure.
 - Maximum allowable change in the pass band gain, A_{max} .
 - Minimum allowable attenuation in the stop band, A_{min} .
 - Cut off Frequency, f_c .
 - Frequency at which the stop band begins, f_s .
- Two possible responses within the desired limits are shown but there are infinite possible responses. **So how to choose the best one?**




Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.




Low Pass Filter (Passive)

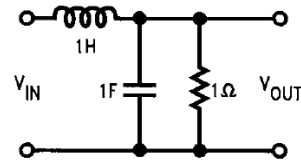- Passes all the frequencies lower than the cut off frequency, f_c , while stopping all the frequencies above the cut off.



- A passive low pass filter is shown in the figure using inductor, capacitor and resistor.
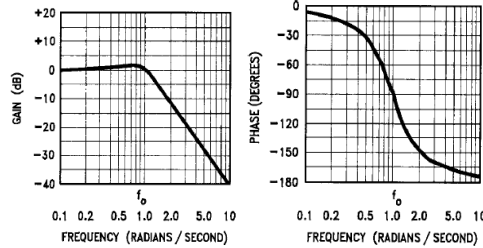
$$H_{LP}(s) = \frac{V_{OUT}}{V_{IN}} = \frac{1}{s^2 + s + 1}$$





Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Low Pass Filter (Active) 1st Order

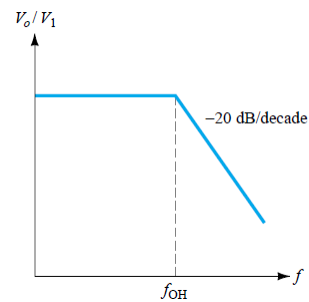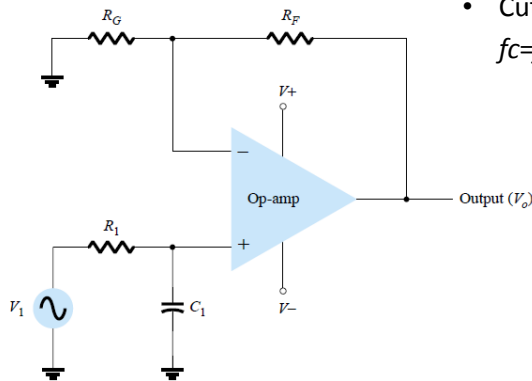- Voltage Gain= $1 + (R_f/R_G)$
- Cut off frequency, f_c or f_{OH}
 $f_c=f_{OH}= 1/(2\pi R_1 C_1)$





Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Low Pass Filter (Active) 2nd Order

- Voltage Gain= ?
- Cut Off Frequency= ?

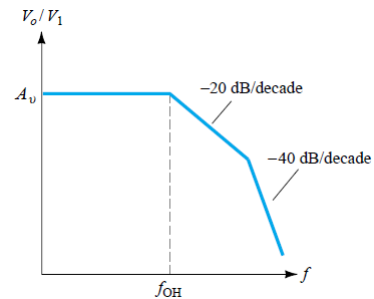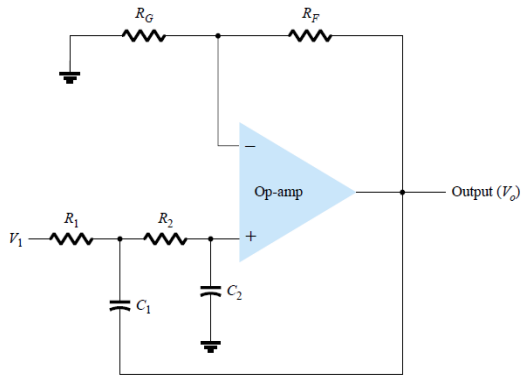

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc., ISBN: 81-7808-590-9.





Low Pass Filter

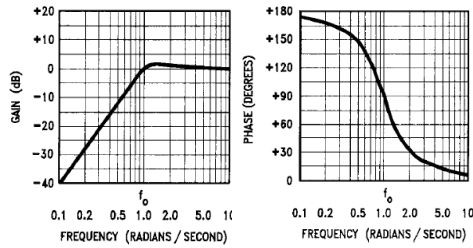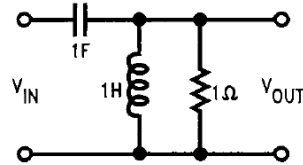- *Example 15.12 (Boylestad):*
Calculate the cut off frequency of a low pass filter with $R_1 = 1.2\text{k}\Omega$ and $C_1 = 0.02\mu\text{F}$.



High Pass Filter (Passive)

- The high pass filter is opposite of low pass filter . This implies that it passes the frequencies above the cut off frequency, f_c , while blocks all the frequencies below f_c .
- The simplest passive high pass filter can be made by interchanging the capacitor and inductors in the low pass filter configuration studied earlier.




$$H_{HP}(s) = \frac{V_{OUT}}{V_{IN}} = \frac{s^2}{s^2 + s + 1}$$

Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.




High Pass Filter (Active)

1st Order

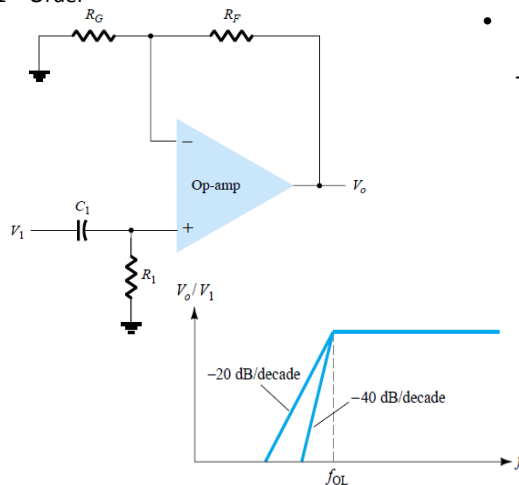

- Cut off Frequency, f_c or f_{OL}
 $f_c = f_{OL} = 1/(2\pi R_1 C_1)$
 Gain = ?

2nd Order

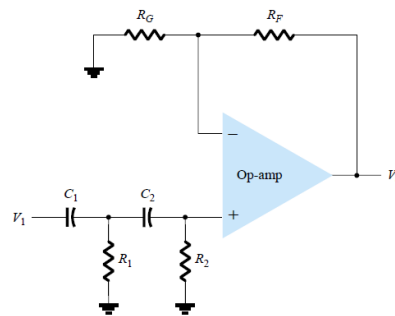

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



High Pass Filter

- *Example 15.13 (Boylestad):*



Next Lecture

- Band Pass Filter.
- Band Stop Filter.



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3
- [3] Kerry Lacanette. Application Note 779: A Basic Introduction to Filters-Active, Passive and Switched Capacitor, Texas Instruments, Literature Number: SNOA224A, April 2010 .
URL to fulltext: <http://www.ti.com/lit/an/snoa224a/snoa224a.pdf>