



# Electronics II

## Lecture 22 Oscillators I

Muhammad Tilal  
Department of Electrical Engineering  
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



# Previous Lecture

- Classic Filter Functions
  - Butterworth.
  - Chebyshev I & II.
  - Elliptic.
  - Bessel.




## Session Overview

<b>Topic</b>	Oscillators.
<b>Concepts</b>	Positive Feedback, Negative Feedback, Oscillators, Barkhausen Criterion, RC Phase Shift Oscillator.
<b>Recommended Reading</b>	Section 17.1, 17.2 & 17.5 of [1]. Section 12-3 of [2].
<b>Keywords</b>	Feedback, Amplifiers, Oscillators, Positive Feedback, Negative Feedback, Oscillator, Barkhausen, Loop Gain, RC Phase Shift.


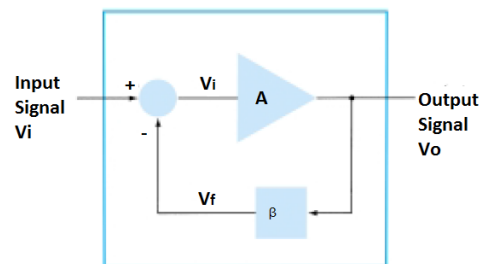
## Feedback

- Feedback is *'returning a portion of the output signal to the input so as to change the performance characteristics of the device'*.
- There are two types of feedback, depending upon the relative polarity of the of the signal being fed back.
  - Negative Feedback.
  - Positive Feedback.
- Negative Feedback
  - When the feedback causes the changes to reduce, it is referred to as the negative feedback. For amplifiers with negative feedback, the gain reduces as a result of feedback.
- Positive Feedback
  - Positive feedback drives a circuit into oscillations.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*,  
8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.


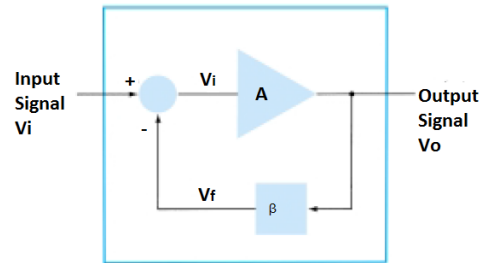
## Negative Feedback

- If the feedback signal is of opposite polarity to the input signal, the feedback is termed as '*negative feedback*'.
- With the negative feedback certain improvements are achieved which include
  - Higher Input Impedance.
  - Better Stabilized Voltage Gain.
  - Improved Frequency Response.
  - Lower Output Impedance.
  - Reduced Noise.
  - More Linear Operation.
- Negative feedback reduces the overall voltage gain.
- For amplifiers, negative feedback is used.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




## Feedback Connection Types

- There are four basic types of feedback connection depending upon the feedback parameter and connection topology.
- These types include
  - Voltage Series Feedback.
  - Voltage Shunt Feedback.
  - Current Series Feedback.
  - Current Shunt Feedback.
- Feedback voltage refers to the output voltage as input to the feedback.
- Feedback current refers to tapping off some output current the feedback network.
- Series refers to connecting the feedback signal in series with the input signal voltage.
- Shunt refers to connecting the feedback signal in parallel with an input current source.
- Series feedback tends to increase the input resistance, while shunt feedback decreases the input resistance.
- Voltage feedback tends to decrease the output impedance while current feedback tends to increase the output impedance.
- Which one of the four types is preferred and why?



## Feedback Connection Types

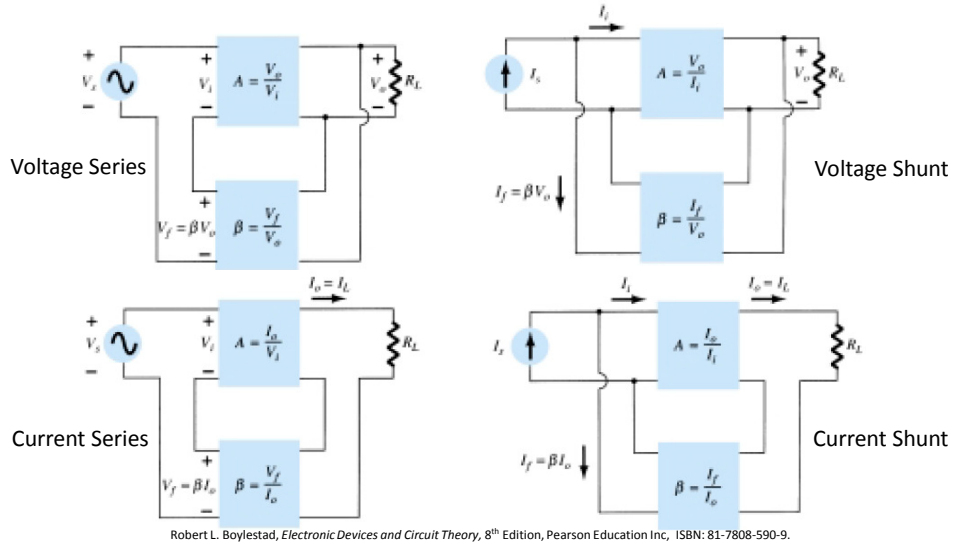

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



## Gain with Feedback

**TABLE 18.1** Summary of Gain, Feedback, and Gain with Feedback from Fig. 18.2

		Voltage-Series	Voltage-Shunt	Current-Series	Current-Shunt
Gain without feedback	$A$	$\frac{V_o}{V_i}$	$\frac{V_o}{I_i}$	$\frac{I_o}{V_i}$	$\frac{I_o}{I_i}$
Feedback	$\beta$	$\frac{V_f}{V_o}$	$\frac{I_f}{V_o}$	$\frac{V_f}{I_o}$	$\frac{I_f}{I_o}$
Gain with feedback	$A_f$	$\frac{V_o}{V_s}$	$\frac{V_o}{I_s}$	$\frac{I_o}{V_s}$	$\frac{I_o}{I_s}$

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc., ISBN: 81-7808-590-9.




## Oscillator Operation

- A device which generates a periodic ac output signal without any form of input signal.
- Oscillation is a form of instability caused by feedback that reinforces a signal that would diminish otherwise due to energy loss.
- Oscillator is a term mostly used for sine-wave signal generator whereas a square wave generator is usually termed as a multi-vibrator.
- For this feedback to be regenerative, there are certain amplitude and phase conditions that must be fulfilled.
- Desirable features of a sine wave oscillator are
  - Low distortion sinusoidal waveform
  - Adjustable frequency range.
- Oscillators are designed with the known feedback characteristics.





## The Barkhausen Criterion

- In the block diagram, A is the amplifier gain while  $\beta$  is the feedback gain.
- Reactive elements especially the capacitors cause the shift in the gain magnitude and phase shift in amplifiers/ oscillators as a function of frequency.
- In order to make the given system work as an oscillator, the loop gain must satisfy the Barkhausen criterion which is
  - $|A\beta|=1$ .
- In general, there exists only one frequency at which the gain magnitude is unity and total phase shift is 0 degrees.
- It is also important to note that not only the gain magnitude must be unity but the in phase signal reinforcement must also occur.

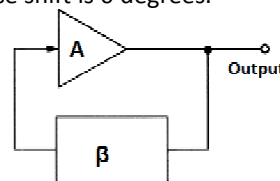



## Oscillator Function

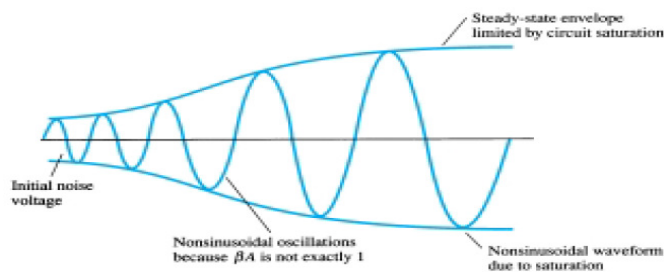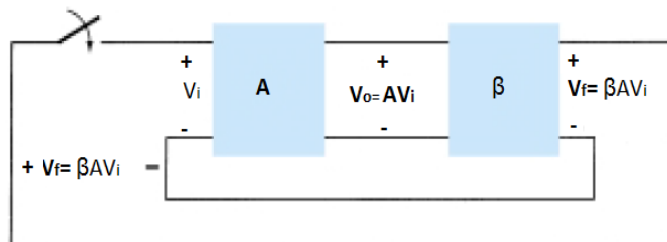

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



## The Barkhausen Criterion

- *Example 12-5 (Bogart)*: The gain of a certain amplifier as a function of frequency is  $A(j\omega) = -16 \times 10^6 / j\omega$ . A feedback path connected around it has  $\beta(j\omega) = 10^3 / (2 \times 10^3 + j\omega)^2$ . Will the system oscillate? If so, at what frequency.

*Solution:*




## Types of Oscillators

- Four basic oscillator configurations will be covered which include
  - RC Phase Shift Oscillator.
  - Wien Bridge Oscillator.
  - Collpits Oscillator.
  - Hartley Oscillator.


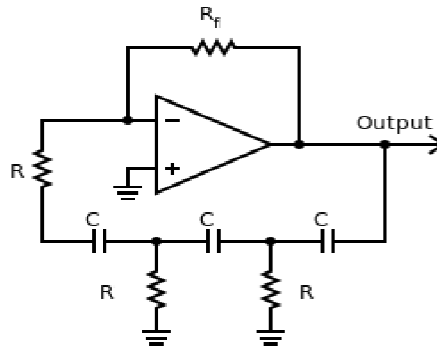
## RC Phase Shift Oscillator

- RC phase shift oscillator is the simplest oscillator using an op-amp in the inverting configuration ( $180^\circ$  phase shift).
- The op-amp drives three cascaded RC sections with  $180^\circ$  phase shift. Thus the total phase shift around the loop is  $360^\circ$ .
- An important point here is that the total phase shift by three cascaded RC sections is equal to  $180^\circ$ .
- The loss in the RC network is compensated by the op-amp gain that is  $v_o/v_i = - (R_f/R)$ .






## RC Phase Shift Oscillator

- $\beta = R^3 / [ (R^3 - 5RXC^2) + j(XC^3 - 6R^2XC) ]$

- $f_o = 1 / 2\pi RC\sqrt{6}$

- $R_f/R_1 = 29$

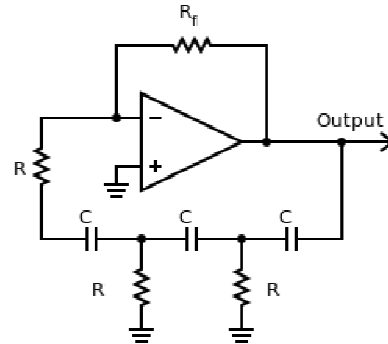


Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6<sup>th</sup> Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



## RC Phase Shift Oscillator

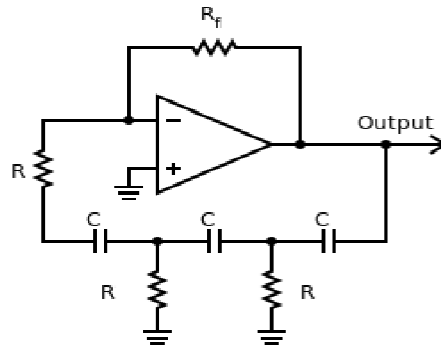- *Example 12-6 (Bogart):* Design an RC Phase shift oscillator capable of oscillation at 100Hz.



Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6<sup>th</sup> Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3





## Next Lecture

- The next lecture will cover the following topics
  - Wien Bridge Oscillator.
  - Collpits Oscillator.
  - Hartley Oscillator.
  - Oscillator Applications.



## References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8<sup>th</sup> Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6<sup>th</sup> Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3