



Electronics II

Lecture 23 Oscillators II

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



Previous Lecture

- Basic structure and operation of oscillator circuit
 - Barkhausen Criterion.



Session Overview

Topic	Oscillators.
Concepts	RC Phase Shift Oscillator, Wien Bridge Oscillator.
Recommended Reading	Sections 17.6 & 17.7 of [1]. Section 12-3 of [2].
Keywords	Oscillator, RC Phase Shift, Wien Bridge.




Types of Oscillators

- Four basic oscillator configurations will be covered which include
 - RC Phase Shift Oscillator.
 - Wien Bridge Oscillator.
 - Collpits Oscillator.
 - Hartley Oscillator.



RC Phase Shift Oscillator

- RC phase shift oscillator is the simplest oscillator using an op-amp in the inverting configuration (180° phase shift).
- The op-amp drives three cascaded RC sections with 180° phase shift. Thus the total phase shift around the loop is 360° .
- An important point here is that the total phase shift by three cascaded RC sections is equal to 180° .
- The loss in the RC network is compensated by the op-amp gain that is $v_o/v_i = -(R_f/R)$.

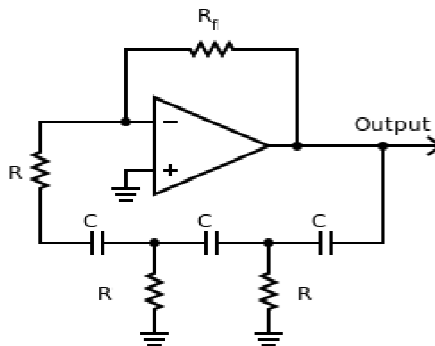


Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



RC Phase Shift Oscillator

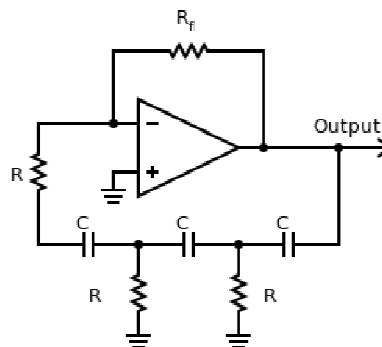- $\beta = R^3 / [(R^3 - 5RXC^2) + j(XC^3 - 6R^2XC)]$
- $f_o = 1 / 2\pi RC\sqrt{6}$
- $R_f/R_1 = 29$




Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



RC Phase Shift Oscillator

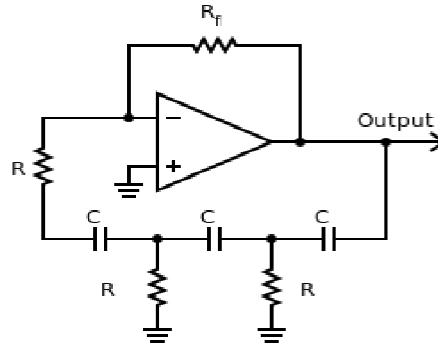- *Example 12-6 (Bogart):* Design an RC Phase shift oscillator capable of oscillation at 100Hz.




Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



Wien-Bridge Oscillator

- Wien bridge oscillator employs an op-amp in non-inverting configuration and two impedance blocks Z_1 and Z_2 forming a voltage divider.
- R_f and R_g determine the amplifier gain and these are selected to make the magnitude of the loop gain equal to 1.
- Amplifier is non inverting so choosing the feedback impedance such that there is 0° phase shift in the signal fed back to the non-inverting input can make the total phase shift of 0° .

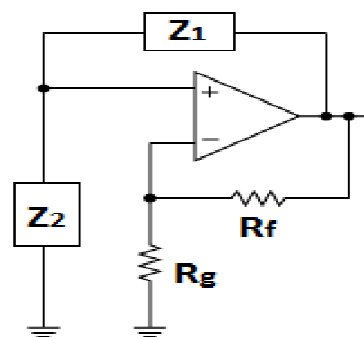

Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



Wien-Bridge Oscillator


- The most common WB oscillator uses series RC combination for Z_1 and parallel RC combination for Z_2 .
- $R_f/R_g = 2$

- $Z_1 = R_1 - jX_{C1}$
- $Z_2 = -(jR_2X_{C2})/(R_2 - jX_{C2})$

- $\beta =$

- $\omega_0 =$

- $f_0 =$

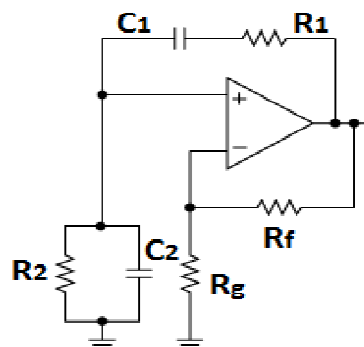


Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



Wien-Bridge Oscillator

- Example 12-7 (Bogart):* Design a Wien Bridge oscillator that oscillates at 25 kHz.

Solution:

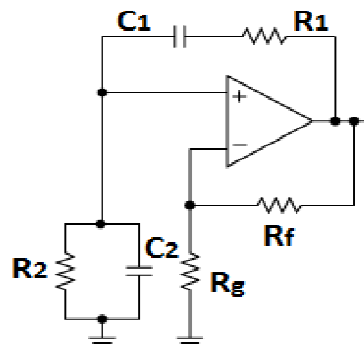


Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, Electronics Devices and Circuits, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



Wien Bridge Oscillator

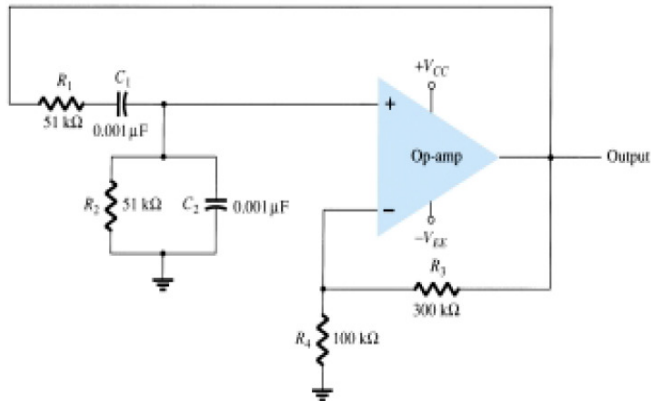- *Example 18.8 (Boylestad):* Calculate the Resonant Frequency of the given oscillator.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



Wien Bridge Oscillator

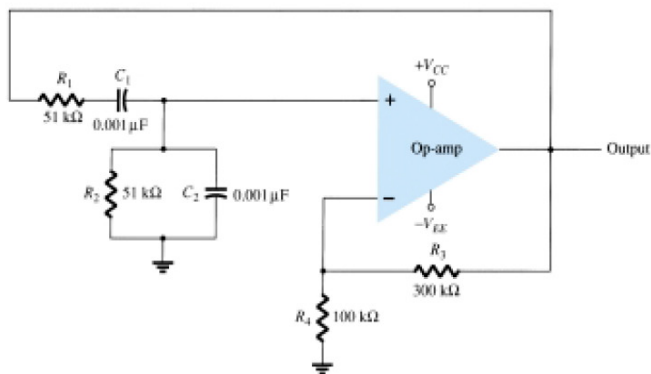- *Example 18.9(Boylestad):* Design a Wein Bridge Oscillator for the resonant frequency of 10kHz .




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc., ISBN: 81-7808-590-9.



Wien-Bridge Oscillator- Practical Considerations

- R_G will not be exactly equal to R_f and same is the case with C_1 and C_2 because of component tolerance.
- Also amplifier is not ideal causing v_- not exactly equal to v_+ .
- The solution to this problem is to use variable R_f in order to adjust the gain to meet the required Barkhausen criterion. This is applicable in laboratory circuits.
- Practical oscillators incorporate a nonlinear device in the feedback loop to provide automatic adjustment of the loop gain to sustain the oscillations. This is termed as *Automatic Gain Control (AGC)*.

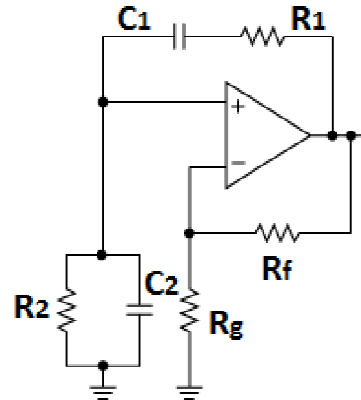

Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3



Next Lecture

- The next lecture will cover the following topics
 - Voltage Comparators.
 - Basics of 555 Timer IC.



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3