



Electronics II

Lecture 24
555 Timer IC

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



Previous Lecture

- Types of Oscillator Circuits
 - Wien Bridge Oscillator.
 - Colpitts Oscillator.
 - Hartley Oscillator.
 - Crystal Oscillator.




Session Overview

Topic	Voltage Comparator, 555 Timer IC
Concepts	Voltage Comparator. Basic Structure of 555 Timer IC, Astable Operation, Mono Stable Operation.
Recommended Reading	Section 16-6 of [1] Sections 12-1 & 12-2 of [3] Sections 16-1, 16-2 & 16-4 of [2]
Keywords	Voltage Comparator, 555 Timer, Astable, Mono Stable.



Voltage Comparator Basics

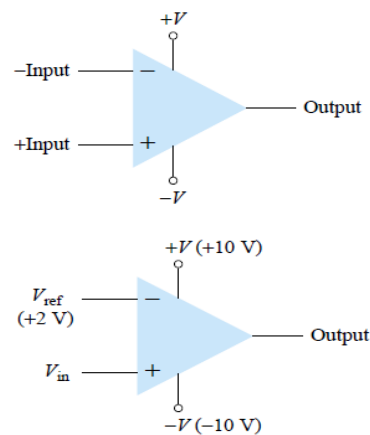- A voltage comparator is a circuit that accepts the linear voltages as inputs and provides a digital output.
- It compares the input voltage levels and its output indicates which of the two inputs is greater.
- The figure shows a comparator configuration when the reference input is given to the inverting input and the non inverting input is connected to V_i .



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition,
Pearson Education Inc., ISBN: 81-7808-590-9.




555 Timer IC- Basic Structure

- 555 timer IC is an analog-digital integrated circuit.
- It consists of
 - linear comparators.
 - A digital flip flop.
 - A resistive voltage divider network.
 - A discharge transistor.
- Linear comparators are devices which provide two level output depending upon the analog input voltage.
- Flip flop is a device which can have two output levels; low and high.
- The resistor voltage divider network is used to set the reference voltages for the comparators.
- The discharge transistor is used to provide a path to the external timing capacitor to discharge.



555 Timer IC- Basic Structure

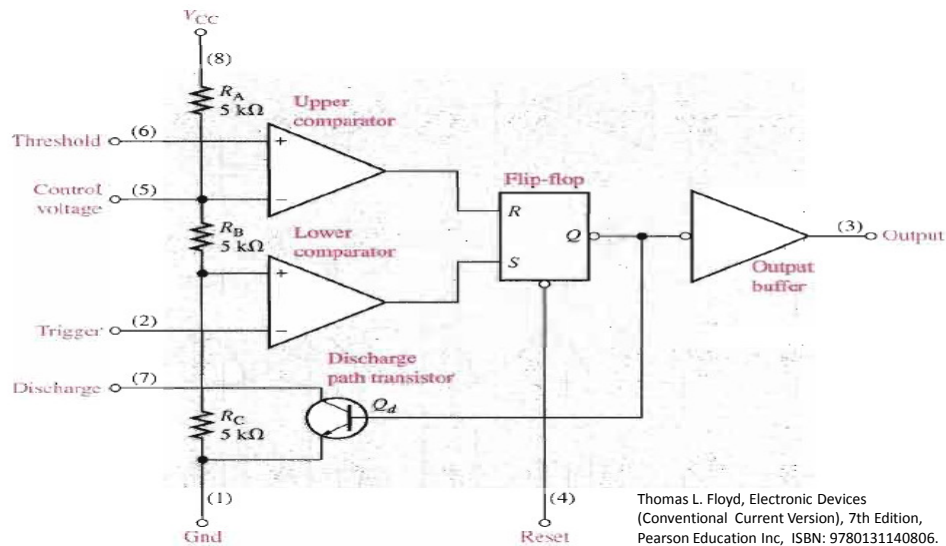




555 Timer IC- Function of Internal Components

- All the resistors in the voltage divider resistive network have equal value.
- Equal resistor values result in the reference levels of $(2/3)V_{CC}$ for the upper comparator and $(1/3)V_{CC}$ for the lower comparator.
- The out put of the comparator controls the flip flop. When the trigger voltage level goes below $(1/3)V_{CC}$, the flip flop is set with a high output.
- The threshold input is connected to the external RC network; when the external capacitor voltage exceeds $(2/3)V_{CC}$, the upper comparator resets the flip flop resulting in the low output.
- When the device output is low, the discharge transistor turns on providing a discharge path for the external timing capacitor.
- With this basic functionality, the timer IC can be configured to work as an oscillator or time delay element etc with the help of external components



555 Timer IC- Modes of Operation


- There are three basic modes of operation of 555 timer IC
 - Astable.
 - Mono-stable.
 - Bi-stable.
- *Astable* mode of operation refers to an operation in which the circuit is not stable in either state. The output continues to switch from one state to another.
- *Mono-stable* mode of operation is when there is one stable state and one unstable state. A trigger pulse causes the circuit to enter the unstable state.
- After entering the unstable state, the circuit remains in that state for a fixed interval of time and then return to the stable state.
- In bi-stable mode of operation the devices have two stable states. Device can enter into any of these two state when triggered by an external pulse.

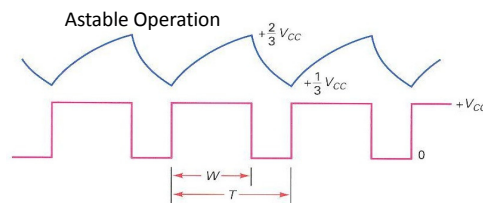

Thomas L. Floyd, Electronic Devices (Conventional Current Version), 7th Edition, Pearson Education Inc, ISBN: 9780131140806.



555 Timer IC- Modes of Operation

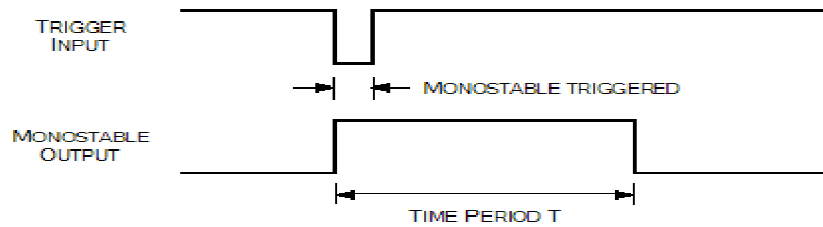


Bistable Mode



555 Timer IC- Astable Operation

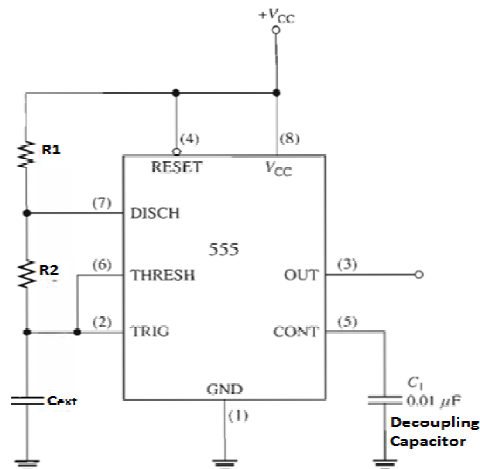
- Also known as 'astable multi-vibrator'.
- Threshold input (THRESH) is connected to the trigger (TRIG) input.
- External components R_1 , R_2 and C_{ext} form the timing circuit that determines the frequency of oscillations.
- The capacitor connected to control (CONT) input is only for decoupling and has no effect on circuit operation.



Thomas L. Floyd, Electronic Devices (Conventional Current Version), 7th Edition, Pearson Education Inc, ISBN: 9780131140806.



555 Timer IC- Astable Operation

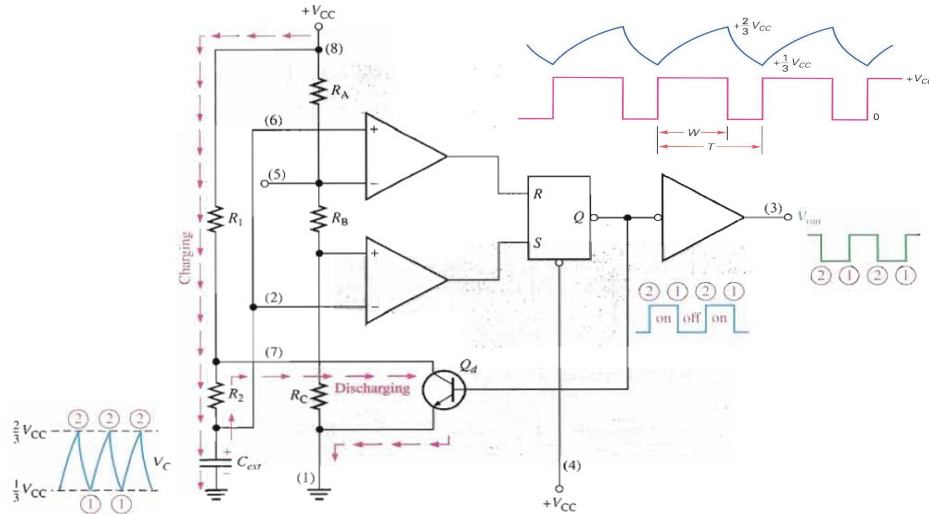

Thomas L. Floyd, Electronic Devices (Conventional Current Version), 7th Edition, Pearson Education Inc, ISBN: 9780131140806.



555 Timer IC- Astable Operation

- Summary of Astable Operation
- Initially C_{ext} is uncharged making the trigger voltage at pin 2 equal to 0V.
- This causes the output of lower comparator to be high and the output of upper comparator to be low.
- This results in high output(Q) of flip flop and low (Q') at base of the discharge transistor.
- C_{ext} starts charging through R1 and R2. When it reaches $(1/3)V_{cc}$, the lower comparator switches to its low output state and when capacitor charges to $(2/3)V_{cc}$ the upper comparator switches to high output state.
- This resets the flip flop causing the transistor to switch on and let the capacitor discharge.
- At a point when capacitor discharges to $(1/3)V_{cc}$, the lower comparator switches high and at $(2/3)V_{cc}$ the upper comparator switches to low turning off the transistor. The cycle continues.




555 Timer IC- Astable Operation

- Frequency of Oscillation
 $f_r = 1.44 / (R_1 + 2R_2)C_{ext}$.
- Total time period
 $T = t_H + t_L = 0.694(R_1 + 2R_2)C_{ext}$.
- Time duration when the output is high (time required by C_{ext} to charge from $(1/3)V_{cc}$ to $(2/3)V_{cc}$)
 $t_H = 0.694(R_1 + R_2)C_{ext}$
- Percent duty cycle
Duty Cycle(D) = $(t_H/T) \times 100\%$
 $D = (t_H / (t_H + t_L)) \times 100\%$
 $D = [(R_1 + R_2) / (R_1 + 2R_2)] \times 100\%$
- Time duration when the output is low (time required by C_{ext} to discharge from $(2/3)V_{cc}$ to $(1/3)V_{cc}$)
 $t_L = 0.694R_2C_{ext}$
- Question: How can we make the duty cycle less than 50 percent?
What will be the new formula for duty cycle less than 50 percent.



555 Timer IC- Astable Operation

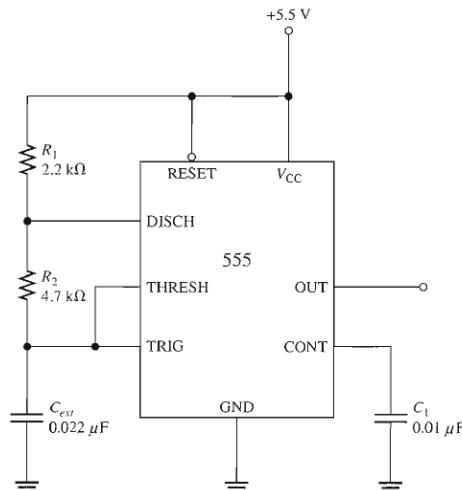- Example 16-6 (Floyd): Determine the Oscillation frequency and duty cycle of the given astable multi-vibrator.



Thomas L. Floyd, Electronic Devices (Conventional Current Version), 7th Edition, Pearson Education Inc, ISBN: 9780131140806.



References

- [1] Thomas L. Floyd, *Electronic Devices (Conventional Current Version)*, 7th Edition, Pearson Education Inc, ISBN: 9780131140806.
- [2] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [3] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3