



Electronics II

Lecture 28

Power Amplifiers II

Class A, Class B & Class AB Amplifiers

Muhammad Tilal

Department of Electrical Engineering
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



Previous Lecture

- Power Amplifiers
 - Basics of Power Amplifiers.
 - Classes of Power Amplifiers.
 - Class A Power Amplifier.



Session Overview

Topic	Power Amplifiers
Concepts	Class A Power Amplifier, Class B Amplifier. Push Pull Circuits, Class AB Amplifiers.
Recommended Reading	Sections 15.2, 15.4 and 15.5(Partial), 15.6 of [1].
Keywords	Power Amplifier, Class A Class B, Class AB, Push-Pull, Push Pull.




Class A Power Amplifier

- Low efficiency but better signal reproduction and linearity.
- In class A amplifier operation, the complete input waveform is reproduced at the output.
- This exact amplified reproduction at the output is possible because the Class A amplifier is perfectly biased within its active region.
- Due to this biasing it never enters the cut-off or saturation region.
- Class A amplifier uses a single transistor for both input cycles. Because of its biasing arrangements, this amplifier always has the current flowing at the output.
- This causes the poor efficiency as the actual power delivered to the load is quite less than the actual power converted.
- Most of the power converted is wasted as heat thereby risking the device burn out if proper sinking is not provided. Additionally, sinks also increase the cost.




Class A Power Amplifier

Class A Output Waveform

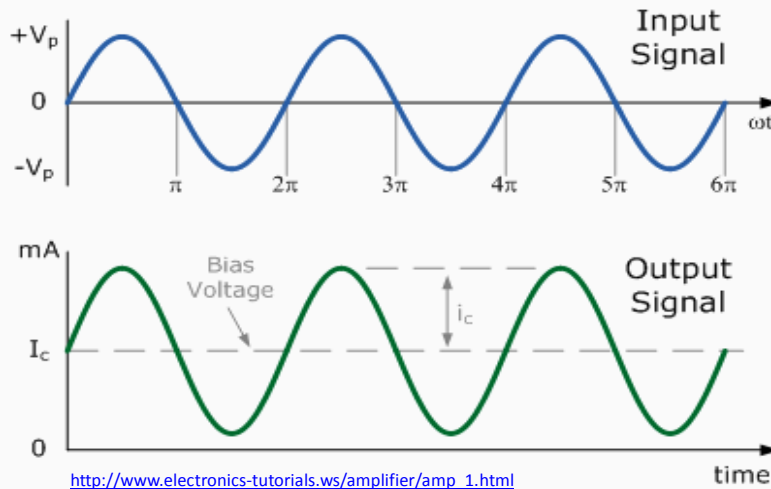

Class A Power Amplifier- AC Operation

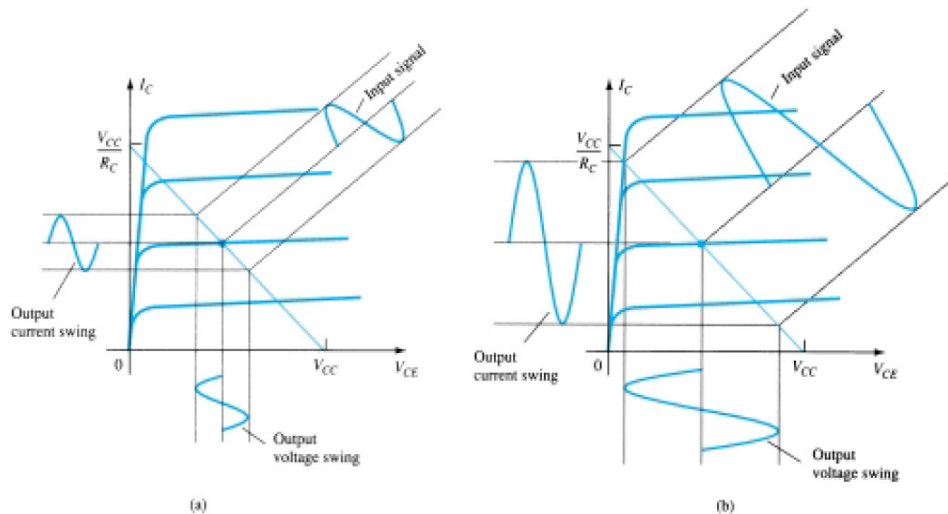

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




Power Considerations- Class A power Amplifier

- Input power is given as
 - $P_{i(dc)} = V_{CC} \cdot I_{CQ}$
- Output power
 - RMS: $P_o(ac) = V_c^2(rms) / R_c$
 - Peak: $P_o(ac) = V_{CE}^2(p) / 2R_c$
 - Peak-Peak: $P_o(ac) = V_{CE}^2(p-p) / 8R_c$
- Efficiency
 - $\% \eta = [P_o(ac) / P_{i(dc)}] \times 100\%$
- Maximum Power Efficiency
 - maximum $V_{CE}(p-p) = V_{CC}$
 - maximum $I_C(p-p) = \frac{V_{CC}}{R_C}$
 - maximum $P_o(ac) = \frac{V_{CC}(V_{CC}/R_C)}{8}$
 - $= \frac{V_{CC}^2}{8R_C}$
 - maximum $P_{i(dc)} = V_{CC}(\text{maximum } I_C)$
 - $= V_{CC} \frac{V_{CC}/R_C}{2} = \frac{V_{CC}^2}{2R_C}$
 - maximum $\% \eta = \frac{\text{maximum } P_o(ac)}{\text{maximum } P_{i(dc)}} \times 100\%$
 - $= \frac{V_{CC}^2/8R_C}{V_{CC}^2/2R_C} \times 100\%$
 - $= 25\%$



Class A Power Amplifier- Example

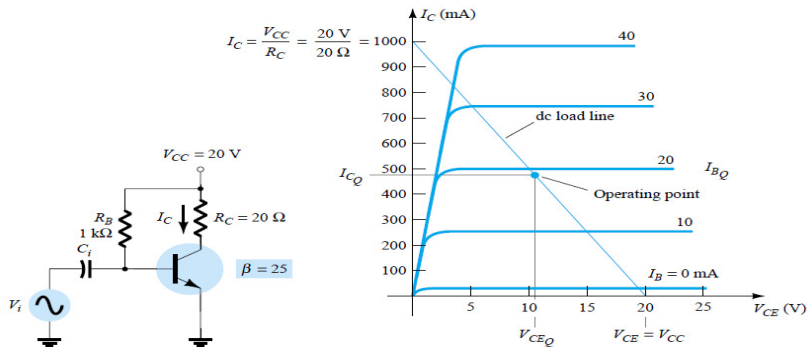
- **Example 15.1 (Boylestad):** Calculate input power, output power and power efficiency of the given power amplifier for input voltage that causes the base current of 10mA peak.





Class B Power Amplifier

- Class B amplifier works only for 180° of output cycle. The DC biasing leaves the transistor turned off when there is not input ac signal.
- To obtain the output for full 360° cycle of operation, two transistor with output at the opposite cycles are coupled together.
- This is termed as the **push-pull configuration**. During one half cycle, one transistor causes the output to be high and during other half cycle, the second transistor causes the output to go low.
- The efficiency of class B amplifier is better than the class A amplifier.
Why ?

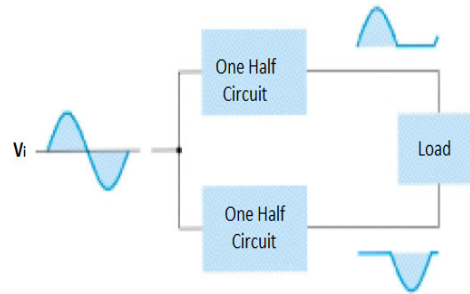


Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Class B Power Amplifier

Class B Output Waveform

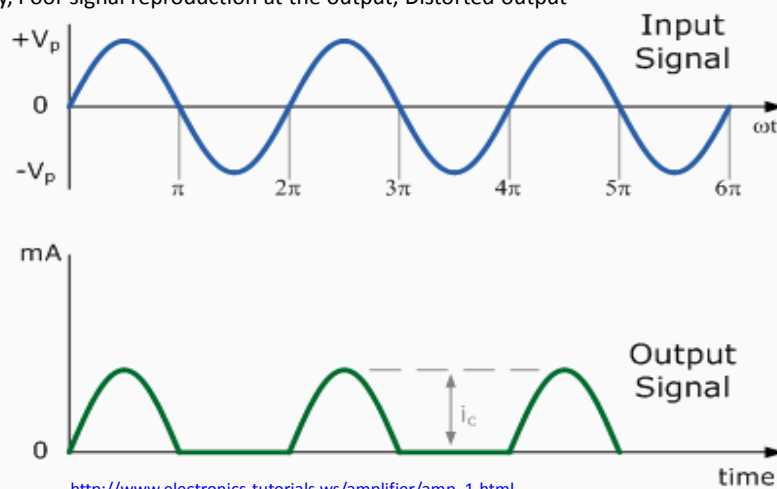Better Efficiency, Poor signal reproduction at the output, Distorted output



http://www.electronics-tutorials.ws/amplifier/amp_1.html



Power Considerations- Class B Power Amplifier


- Input DC power
 - $P_{i(dc)} = V_{CC} \cdot I_{dc}$.
 - I_{dc} = average or DC current.
 - $I_{dc} = (2/\pi) \cdot I_p$.
 - $P_{i(dc)} = V_{CC} \cdot (2/\pi) \cdot I_p$.

- Output AC Power
 - $P_{o(ac)} = V_L^2(\text{rms})/R_L$.
 - $P_{o(ac)} = V_L^2(p-p)/8R_L$.
 - $P_{o(ac)} = V_L^2(p)/2R_L$.

- Efficiency

$$\% \eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100\%$$
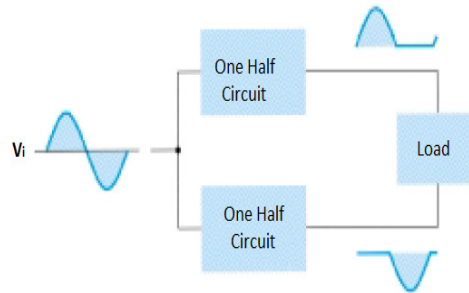
$$\% \eta = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100\% = \frac{V_L^2(p)/2R_L}{V_{CC}[(2/\pi)I(p)]} \times 100\% = \frac{\pi}{4} \frac{V_L(p)}{V_{CC}} \times 100\%$$




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Power Considerations- Class B Power Amplifier

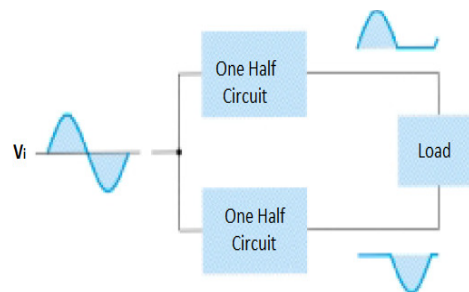- Example 15.7(Boylestad):

For a class B amplifier providing a 20-V peak signal to a 16-Ω load (speaker) and a power supply of $V_{CC} = 30$ V, determine the input power, output power, and circuit efficiency.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Maximum Power Considerations Class B Power Amplifier

- Maximum output power is delivered when $V_{L(p)} = V_{CC}$.
 - Maximum $P_{o(ac)} = V_{CC}^2 / 2R_L$
- Corresponding maximum Peak ac current
 - $I_{(p)} = V_{CC} / R_L$
- Maximum average current from power supply
 - Max $I_{dc} = (2/\pi) I_{(p)} = 2V_{CC}^2 / \pi R_L$
- Maximum input power
 - Max $P_{i(dc)} = V_{CC} * (\text{max } I_{dc})$
 - Max $P_{i(dc)} = 2V_{CC}^2 / \pi R_L$
- Maximum % Efficiency, η
 - $\eta\% = [P_{o(ac)} / P_{i(dc)}] * 100$
 - $\eta\% = \frac{V_{CC}^2 / 2R_L}{V_{CC} [(2/\pi)(V_{CC} / R_L)]} \times 100\%$
 - $\eta\% = \frac{\pi}{4} \times 100\% = 78.54\%$
- Check the formulae for Maximum power dissipated.



Maximum Power Considerations Class B Power Amplifier

- Example 15.8 (Boylestad):
For a class B amplifier using a supply of $V_{CC} = 30 \text{ V}$ and driving a load of 16Ω , determine the maximum input power, output power, and transistor dissipation.



Maximum Power Considerations Class B Power Amplifier

- Example 15.9 (Boylestad):
Calculate the efficiency of a class B amplifier for a supply voltage of $V_{CC} = 24\text{ V}$ with peak output voltages of:
 - (a) $V_L(p) = 22\text{ V}$.
 - (b) $V_L(p) = 6\text{ V}$.

Robert L. Boylestad, *Electronic Devices and Circuit Theory*,
8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.




Class B Power Amplifier Circuit

- There are multiple circuits to obtain a class B power amplifier operation.
- There are many arrangements to split a single input into two opposite polarity signals.
- For a push-pull configuration, one possible method is to split a single input signal into two opposite polarity signals.
- These arrangements include
 - Transformer Coupled Method.
 - BJT Method.
 - Op-amp Method.
- These opposite polarity signals are fed into two similar input circuits (with each operating for alternate cycle) to get a full 360 degrees of operation.
- All these arrangements are known as phase splitter circuits.



Phase Splitter Circuit for Class B PA

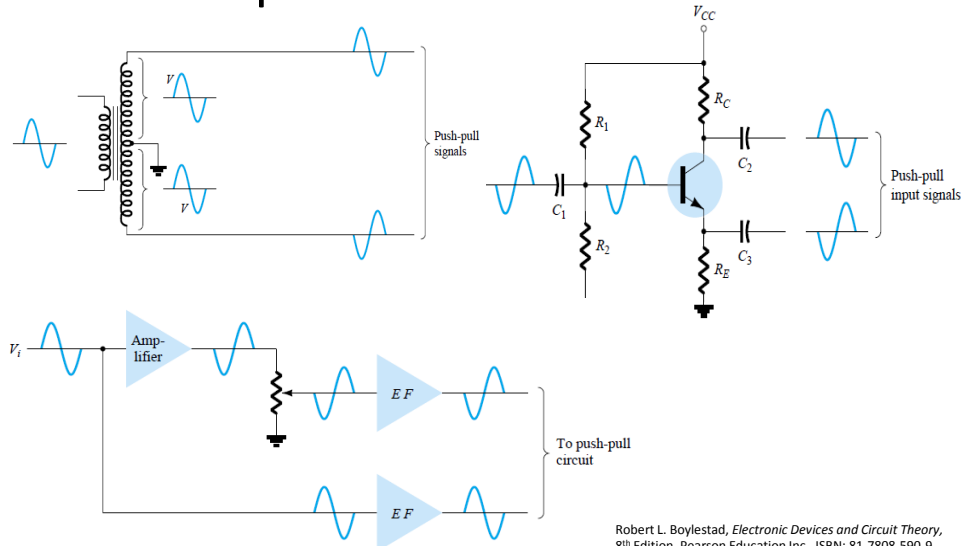


Transformer Coupled Push Pull Circuits

- A transformer splits the input signals into opposite polarity signals which are connected to the input of two transistors.

Output transformer drives the load in push pull fashion.

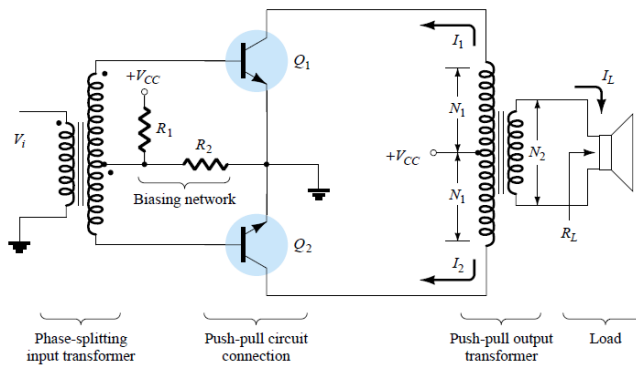
Q1 operates during 1st half cycle and Q2 in 2nd half cycle.



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Complementary Symmetry Circuit

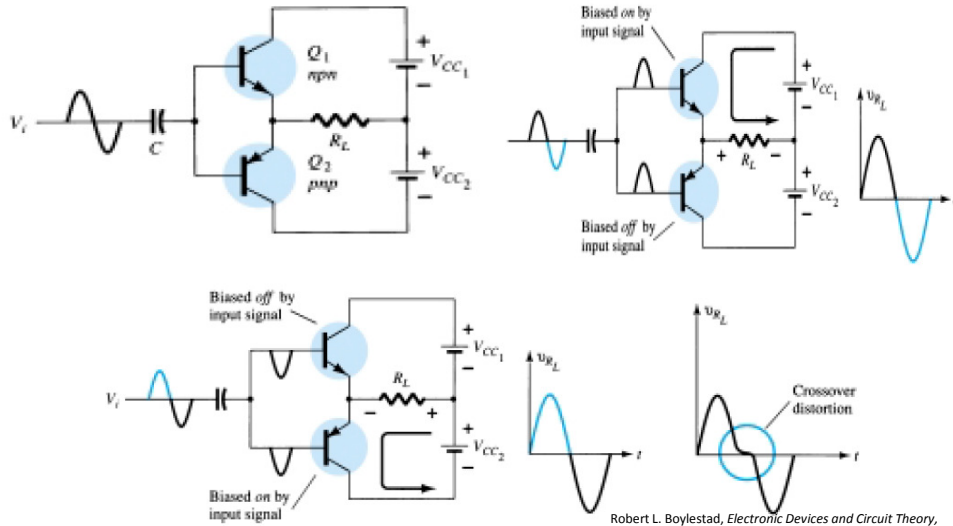


Class AB Power Amplifiers

- Class AB operation is a mode of operation in between Class A and Class B.
- Class AB operation two complimentary transistors biased with very small voltage at the base of the transistors.
- This biasing configuration keep the amplifier close to its cut off state.
- An input AC signal will cause the transistor to operate in its active region.
- In the absence of the input signal, a very small amount of collector current flows thereby preventing any crossover distortion.
- This arrangement causes the efficiency of Class AB better than Class A and removes the cross over distortion present in Class B amplifiers.



Class AB Power Amplifiers

Class AB Output Waveform

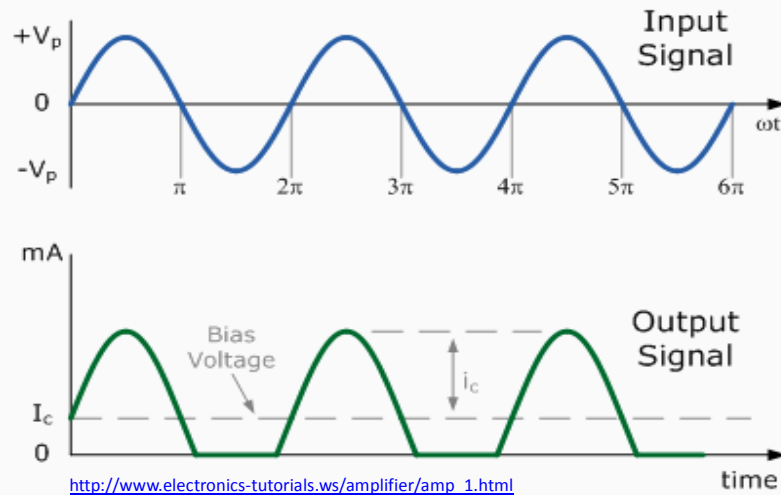

Next Lecture

- Power Amplifiers
 - Amplifier Distortion.
 - Class C Amplifier.
 - Class D Amplifier.



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3