



Electronics II

Lecture 04
re Equivalent Model for
Common Base & Common Emitter

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited. The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden.



Previous Lecture

- Important Amplifier Parameters using Two Port System
 - Voltage Gain.
 - Current Gain.
- re Equivalent Model for
 - Common Base Configuration.




Session Overview

Topic	re Model for Common Base, Common Emitter & Common Collector configurations.
Concepts	re model for Common Base & Common Emitter
Recommended Reading	Section 7.5 of [1]
Keywords	re Model, Common Base, Common Emitter.



Common Base Configuration

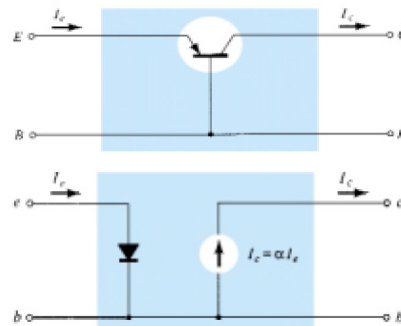
- A pnp transistor is employed to derive the r_e model for common base configuration.
- It is depicted in a way to replicate the two port network.
- The forward biased pn junction is replaced by a diode.
- A current source is connected in order to represent the collector current I_c .
- AC resistance of diode can be determined by
- $r_{ac} = 26\text{mV}/I_D$ $r_e = 26\text{mV}/I_E$



Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Common Base Configuration

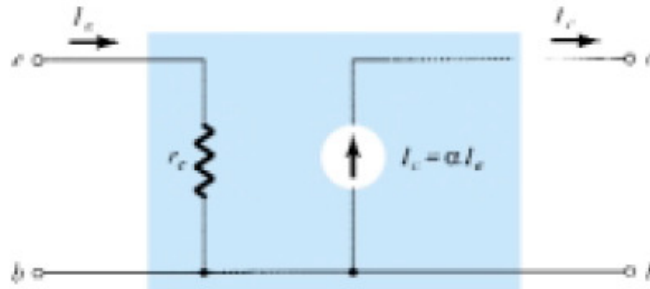

Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Common Base Configuration

- Input Impedance, $Z_i = r_e$.
 - Typical Values are 1 - 50Ω.
- Output Impedance, $Z_o \cong \infty \Omega$.
 - Set input to zero
 - $I_e = 0A$, $I_c = \alpha I_e = 0A$.
 - Typical value: Mega Ohms.
- For common base configuration
 - Input Impedance= Small.
 - Output Impedance= Large.
- Current Gain, $A_i = I_o / I_i = -I_c / I_e$
 $= -\alpha I_e / I_e = -\alpha \cong -1$
- Voltage Gain, $A_v = R_L / r_e$




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Common Base Configuration

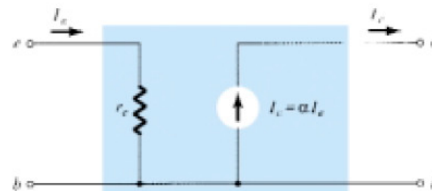- Example 7.4(Boylestad): For the given common base configuration with $I_E=4\text{mA}$, $\alpha=0.98$, ac signal of 2 mV applied between base and emitter terminals, determine
 - Input Impedance.
 - Voltage Gain with $R_L=0.56\text{k}\Omega$.
 - Output Impedance.
 - Current Gain.





Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Common Emitter Configuration

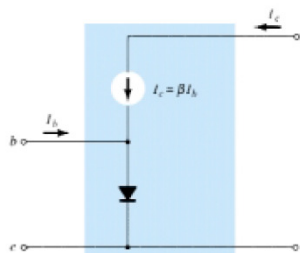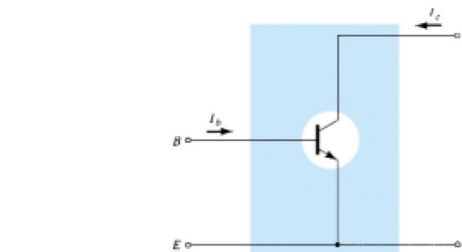- **Input Terminals:** Base and Emitter.
- **Output Terminals:** Collector and Emitter.
- Emitter is common to both the input and the output.
- According to the re equivalent model, a diode is connected between the base and emitter while a current source is connected between the collector and base terminals.
- I_b is the input current and I_c is the output current.




Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.



Common Emitter Configuration

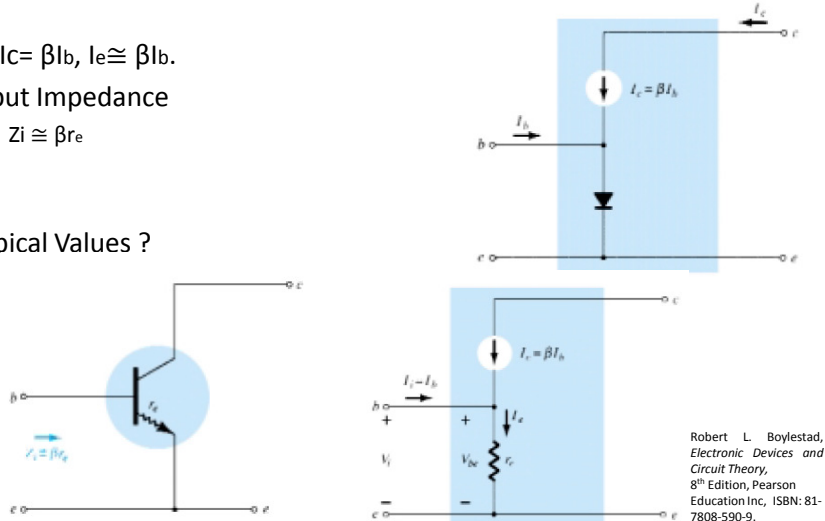- $I_b, I_c = \beta I_b, I_e \cong \beta I_b$.
- Input Impedance
 - $Z_i \cong \beta r_e$
- Typical Values ?



Robert L. Boylestad,
*Electronic Devices and
 Circuit Theory*,
 8th Edition, Pearson
 Education Inc, ISBN: 81-
 7808-590-9.



References

[1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.