



Electronics II

Lecture 18 Filters I

Muhammad Tilal
Department of Electrical Engineering
CIIT Attock Campus

The theme of this presentation is an inspiration from the one used in S2 Department of Chalmers University of Technology, Gothenburg, Sweden. The COMSATS logo and "COMSATS" is the property of CIIT, Pakistan and subject to the copyrights and ownership of COMSATS. Duplication & distribution of this work for Non Academic or Commercial use without prior permission is prohibited.



Previous Lecture

- Operational Amplifier
 - Inverting and non inverting amplifiers.
 - Summing and Subtraction Circuits using Op-amp
 - Op amp Integrator.



Session Overview

Topic	Filters
Concepts	Basic Filter Concepts, Low Pass Filter, High Pass Filter, Band Pass Filters, Band Stop Filters, Filter Parameters.
Recommended Reading	Section 14-6 of [1] Section 11-5 of [2] Sections 1.0, 1.1, 1.4 of [3]
Keywords	Active Filters, Low Pass, High Pass, Band Pass, Band Stop.




Some important Concepts

- Some important concepts must be reviewed before starting the topic. These are
- **Frequency:** Frequency can be mentioned in 'Hertz' or 'Radians per second'.
- **Decibels (dB):** Gain can be specified in 'dB' or 'linear' scale. $Voltage\ gain\ (dB) = 20\log(V_o/V_{in})$.
- **Phase:** Phase can be specified in 'Degrees' or 'Radians'.
- Other concepts include
 - Poles.
 - Zeros.
 - Bode Plots.
 - Magnitude Response.
 - Phase Response.
 - Bandwidth.
 - Cut off Frequency.
 - Pass Band.
 - Stop Band.



Filters

- A filter is a device that allows signals with specific frequencies to pass through it while attenuating all the other signals.
- In other words a filter will neither add any new frequencies to the signal nor change the component frequencies but it will only change the amplitude and phase components w.r.t. certain frequencies.
- Generally, filter has a gain which is dependent on the frequencies (An elaboration of this point will be made in a later portion of the lecture).

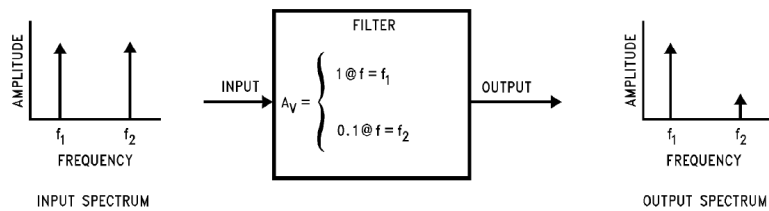

Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Filter Response

- Generally, filters are defined by their frequency domain effects so most analytical and graphical description of filter characteristics are done in frequency domain.
- Typical curves include
 - Gain vs Frequency.
 - Phase vs Frequency.
- Mathematically, frequency domain behavior of the filter is described by 'transfer function' or 'network function'.
- Transfer function is ratio of the Laplace transforms of output and input signals.
- Voltage transfer function can be written as
 - $H(s) = V_{out}(s) / V_{in}(s)$
 - Where $V_{out}(s)$ = Output voltage.
 - $V_{in}(s)$ = Input voltage.
 - s = complex frequency variable.
- The filter transfer function defines the filter's response to any arbitrary signal.
- But mostly the filter response to the sinusoids is required.
- Transfer function can be subdivided into two categories namely amplitude response and phase response.



Filter Response

Amplitude Response

- The transfer function magnitude response vs frequency is *amplitude* or (sometimes called) *frequency* response of the filter.
- It provides information on filter's ability to distinguish between the frequencies.
- $|H(j\omega)| = |V_{out}(j\omega)/V_{in}(j\omega)|$

Phase Response

- Phase response represents the amount of phase shift introduced in the sinusoidal signals as a function of frequency.
- Phase shift is very important when dealing with the complex signals where timing relationship between different signal components is critical.
- $\arg H(j\omega) = \arg(V_{out}(j\omega)/V_{in}(j\omega))$



Classification on the Basis of Circuitry

Passive Filters

- Passive filters are constructed using passive components which include resistors, capacitors and inductors.
- Passive filters have following advantages
 - Simple to implement (only low order).
 - Require no power supplies.
 - Have no bandwidth limitations.
- Passive filters have following disadvantages
 - Have thermal noise.
 - No signal gain.
 - Higher order filters need complex design (inaccurate and expensive)

Active Filters

- Active filters employ active components such as transistors and operational amplifiers along with resistors and capacitors.
- Active filters have following advantages
 - Accurate desired parameters (Input and output impedances).
 - Provide gain.
- Active filters have following disadvantages
 - Limited bandwidth.
 - Require power supplies.
 - Also generate noise.



Classification on the Basis of Design Types

(Only two are considered here)

Butterworth

- Also called maximally flat filter because of less gain variation in the pass band.
- Gain falls at less steeper rate outside pass band.
- Frequency response within the pass band is closer to the ideal filter.

Chebyshev


- Chebyshev has more gain variation in the pass band.
- Gain falls at a steeper rate outside pass band.
- Frequency response outside pass band is closer to the ideal filter.



Classification on the Basis of Allowed Frequencies


Low Pass Filter

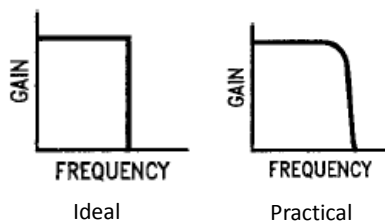- Passes all the frequencies below the cut off frequency and blocks all the frequencies above the cut off frequency.



High Pass Filter

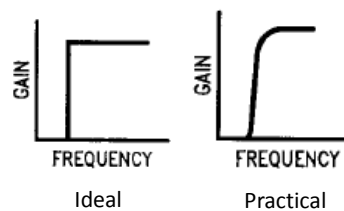- Passes all the frequencies above the cut off frequency while blocks all the frequencies below the cut off frequency.




Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.




Classification on the Basis of Allowed Frequencies

Band Pass Filter

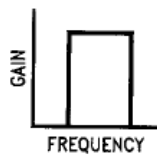- Passes all the frequencies within certain specified range of frequencies within upper cut off and lower cutoff frequencies.




Ideal

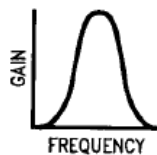


Practical

Band Stop Filter Filter

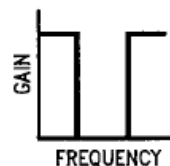- Stops all the frequencies within certain specified range of frequencies.



Ideal

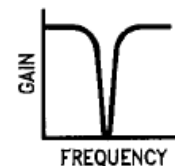

Practical

Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Filter Approximations and Properties

- The ideal filter is characterized by very sharp transition between the pass band and the stop band.
- This approximation to the ideal filter depends upon our goal and certain properties are important in this regard.
- The ideal filter response separates the filter response between the two bands perfectly.
- These properties include
 - Filter order.
 - Ultimate roll off rate.
 - Attenuation rate near the cut off frequency.
 - Transient response.
 - Monotonicity.
 - Pass band ripple.
 - Stop band ripple.
- Practically, the ideal response is not physically realizable but the filter response can be made closer to the ideal.



Filter Properties

Filter Order

- Filter order is of prime importance because it is directly related to the number of components used to design a filter.
- So filter order indirectly influences the cost, physical size and complexity of design.
- Higher order filters are expensive, take more space and complex to design.
- Higher order filters are better!
Why?

Ultimate Roll Off

- Usually expressed as amount of attenuation in dB for a given ratio of frequencies.
- Most common units include dB/octave and dB/decade. (octave? decade?)
- Different filters have different attenuation slopes and depends on the specific design.




Filter Properties

Attenuation Rate near the Cut Off Frequency

- It is the rate at which the filter response drops near the cut off frequency.
- If the frequency to be passed and frequency to be stopped are very close, a larger attenuation rate near the cut off is required.

Transient Response

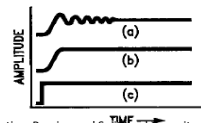- Amplitude response show the filter behavior to the steady state sinusoidal input signals.
- Practically much complex signals can be applied to the filter input so the transient response must be considered.





Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



Filter Properties

Monotonicity

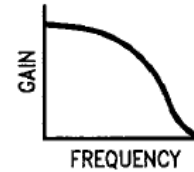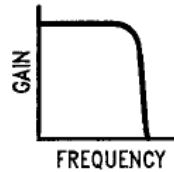- A filter has a monotonic amplitude response if its gain slope never changes sign.
- This implies that gain always increases with the increasing frequency or always decreases with the increasing frequency.
- This is applicable only in high pass and low pass filters whereas band pass and band stop cannot have this property for their total bandwidth.



Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments Inc.



References

- [1] Robert L. Boylestad, *Electronic Devices and Circuit Theory*, 8th Edition, Pearson Education Inc, ISBN: 81-7808-590-9.
- [2] Theodore F. Bogart, Jeffery S. Beasley, Guillermo Rico, *Electronics Devices and Circuits*, 6th Edition, Pearson Education Inc, ISBN: 978-81-775-8887-3
- [3] Kerry Lacanette. Application Note 779: A Basic Introduction to Filters- Active, Passive and Switched Capacitor, Texas Instruments, Literature Number: SNOA224A, April 2010 .
URL to fulltext: <http://www.ti.com/lit/an/snoa224a/snoa224a.pdf>